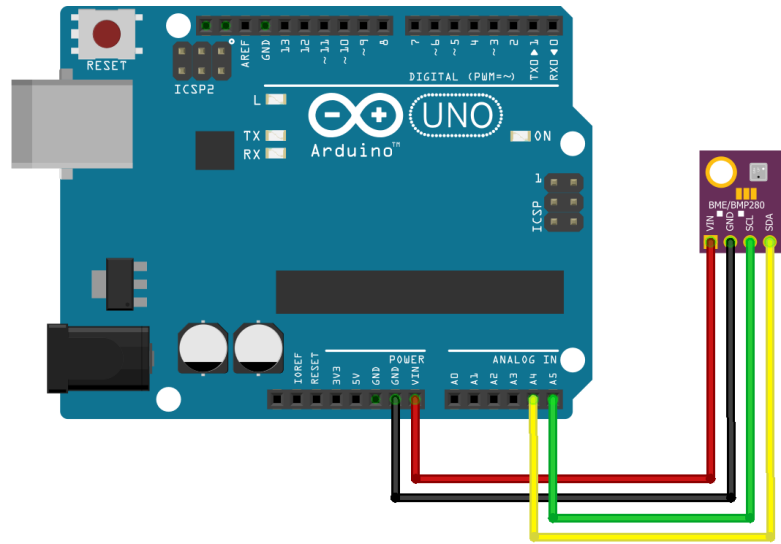# INTERFACING BME280 WITH ARDUINO UNO R3

Schematic Diagram:

fritzing